

GEORGIA INSTITUTE OF TECHNOLOGY
SCHOOL OF ELECTRICAL AND COMPUTER ENGINEERING

ECE 3040: Microelectronic Circuits

Homework #6

Homework Due Date: Monday, March 9, 2026

1. Pierret, Problem 10.3 (20 points)
2. Pierret, Problem 10.10 (20 points)
3. Pierret, Problem 11.2 (a)-(d) (20 points)
4. Pierret, Problem 11.8 (a)-(d) (20 points)

5. BJT: Currents (20 points)

The schematic below represents the current components in a $p^{+}np$ BJT. Draw an equivalent schematic for an $n^{+}pn$ transistor.

